# Model reduction of nonlinear circuit equations

Tatjana Stykel

Technische Universität Berlin

Joint work with T. Reis and A. Steinbrecher





BIRS Workshop, Banff, Canada, October 25-29, 2010

### Outline

- Differential-algebraic equations in circuit simulation
- Model order reduction problem
- PAssivity-preserving Balanced Truncation method for Electrical Circuits (PABTEC)
  - Decoupling of linear and nonlinear parts
  - Model reduction of linear equations
  - Recoupling
- Numerical examples
- Conclusion

T. Stykel. Model reduction of nonlinear circuit equations - p.1

#### **Modified Nodal Analysis (MNA)**



 $\mathbf{A} = [A_{\mathcal{R}}, A_{\mathcal{C}}, A_{\mathcal{L}}, A_{\mathcal{V}}, A_{\mathcal{I}}]$ 

Kirchhoff's current law:  $\mathbf{A}j = 0, \quad j = \begin{bmatrix} j_{\mathcal{R}}^T, \ j_{\mathcal{L}}^T, \ j_{\mathcal{L}}^T, \ j_{\mathcal{V}}^T, \ j_{\mathcal{I}}^T \end{bmatrix}^T$ Kirchhoff's voltage law:  $\mathbf{A}^T \eta = v, \quad v = \begin{bmatrix} v_{\mathcal{R}}^T, \ v_{\mathcal{C}}^T, \ v_{\mathcal{L}}^T, \ v_{\mathcal{V}}^T, \ v_{\mathcal{I}}^T \end{bmatrix}^T$ Branch constitutive relations:

resistors: 
$$j_{\mathcal{R}} = g(v_{\mathcal{R}}), \qquad \mathcal{G}(v_{\mathcal{R}}) = \frac{\partial g(v_{\mathcal{R}})}{\partial v_{\mathcal{R}}}$$
  
capacitors:  $j_{\mathcal{C}} = \frac{dq(v_{\mathcal{C}})}{dt}, \qquad \mathcal{C}(v_{\mathcal{C}}) = \frac{\partial q(v_{\mathcal{C}})}{\partial v_{\mathcal{C}}}$   
inductors:  $v_{\mathcal{L}} = \frac{d\phi(j_{\mathcal{L}})}{dt}, \qquad \mathcal{L}(j_{\mathcal{L}}) = \frac{\partial\phi(j_{\mathcal{L}})}{\partial j_{\mathcal{L}}}$ 

T. Stykel. Model reduction of nonlinear circuit equations - p.2

#### **MNA circuit equations**

Consider a linear DAE system

$$\begin{aligned} \mathcal{E}(x) \, \dot{x} &= \mathcal{A} \, x + f(x) + \mathcal{B} \, u \\ y &= \mathcal{B}^T x \end{aligned}$$

with

$$\mathcal{E}(x) = \begin{bmatrix} A_{\mathcal{C}} \mathcal{C}(A_{\mathcal{C}}^{T} \eta) A_{\mathcal{C}}^{T} & 0 & 0 \\ 0 & \mathcal{L}(j_{\mathcal{L}}) & 0 \\ 0 & 0 & 0 \end{bmatrix}, \quad \mathcal{A} = \begin{bmatrix} 0 & -A_{\mathcal{L}} & -A_{\eta} \\ A_{\mathcal{L}}^{T} & 0 & 0 \\ A_{\mathcal{V}}^{T} & 0 & 0 \end{bmatrix}, \quad \mathcal{B} = \begin{bmatrix} -A_{\mathcal{I}} & 0 \\ 0 & 0 \\ 0 & -I \end{bmatrix},$$
$$f(x) = \begin{bmatrix} -A_{\mathcal{R}} g(A_{\mathcal{R}}^{T} \eta) \\ 0 \\ 0 \end{bmatrix}, \quad u = \begin{bmatrix} j_{\mathcal{I}} \\ v_{\mathcal{V}} \end{bmatrix}, \quad x = \begin{bmatrix} \eta \\ j_{\mathcal{L}} \\ j_{\mathcal{V}} \end{bmatrix}, \quad y = -\begin{bmatrix} v_{\mathcal{I}} \\ j_{\mathcal{V}} \end{bmatrix},$$

- node potentials,  $\eta$ 

 $j_{\mathcal{L}}, j_{\mathcal{V}}, j_{\mathcal{I}}$  — currents through inductors, voltage and  $v_{\mathcal{V}}, v_{\mathcal{I}}$  — voltages at voltage and current sources, - currents through inductors, voltage and current sources,

 $A_{\mathcal{R}}, A_{\mathcal{C}}, A_{\mathcal{L}}, A_{\mathcal{V}}, A_{\mathcal{I}}$  – incidence matrices of resistors, capacitors, inductors, voltage and current sources

T. Stykel. Model reduction of nonlinear circuit equations

#### Assumptions

- $A_{\nu}$  has full column rank (= no V-loops)
- $[A_{\mathcal{C}}, A_{\mathcal{L}}, A_{\mathcal{R}}, A_{\mathcal{V}}]$  has full row rank (= no l-cutsets)
- **\square \mathcal{C}**,  $\mathcal{L}$ ,  $\mathcal{G}$  are symmetric, positive definite

#### Index characterization [Estévez Schwarz/Tischendorf'00]

- Index = 0 ⇔ no voltage sources and every node has a capacitive path to a reference node
- Index = 1  $\Leftrightarrow$  no CV-loops except for C-loops and no LI-cutsets
- Index = 2, otherwise

T. Stykel. Model reduction of nonlinear circuit equations - p.4

#### **Model reduction problem**

Given a large-scale system  $\mathcal{E}(x) \dot{x} = \mathcal{A} x + f(x) + \mathcal{B} u$   $y = \mathcal{C} x$ with  $x \in \mathbb{R}^n$  and  $u, y \in \mathbb{R}^m$ ,

find a reduced-order system  $\widetilde{\mathcal{E}}(\widetilde{x})\dot{\widetilde{x}} = \widetilde{\mathcal{A}}\widetilde{x} + \widetilde{f}(\widetilde{x}) + \widetilde{\mathcal{B}}u$   $\widetilde{y} = \widetilde{\mathcal{C}}\widetilde{x}$ with  $\widetilde{x} \in \mathbb{R}^r$ ,  $u, \widetilde{y} \in \mathbb{R}^m$ ,  $r \ll n$ .

- preservation of passivity and stability
- Small approximation error  $\|\widetilde{y} y\| \leq tol \|u\|$  for all  $u \in \mathcal{U}$ 
  - $\hookrightarrow$  need for computable error bounds
- numerically stable and efficient methods

T. Stykel. Model reduction of nonlinear circuit equations - p.5

### **Model reduction techniques**

#### Linear circuit equations

- Krylov subspace methods (moment matching)
   SyPVL for RC, RL, LC circuits [Freund et al.'96,'97]
   PRIMA, SPRIM for RLC circuits [Odabasioglu et al.'96,'97; Freund'04,'05]
   Positive real interpolation [Antoulas'05, Sorensen'05, Ionutiu et al.'08]
- Balancing-related model reduction methods
   LyaPABTEC for RC, RL circuits
   PABTEC for RLC circuits
   [Reis/S.'09]

#### Nonlinear circuit equations

- Proper orthogonal decomposition (POD) [Verhoeven'08]
- Trajectory piece-wise linear approach (TPWL)
- (Quadratic) bilinearization + balanced truncation [Benner/Breiten'10]

[Rewieński'03]

T. Stykel. Model reduction of nonlinear circuit equations - p.6

## PABTEC Tool





Large linear RLC circuits arise in

- modelling transmission lines and pin packages
- modelling circuits elements by Maxwell's equations via partial element equivalent circuits (PEEC)

#### Assume that

$$A_{\mathcal{C}} = \begin{bmatrix} A_{\mathcal{C}_l}, & A_{\mathcal{C}_n} \end{bmatrix}, \qquad A_{\mathcal{L}} = \begin{bmatrix} A_{\mathcal{L}_l}, & A_{\mathcal{L}_n} \end{bmatrix}, \qquad A_{\mathcal{R}} = \begin{bmatrix} A_{\mathcal{R}_l}, & A_{\mathcal{R}_n} \end{bmatrix},$$
$$\mathcal{C}(A_{\mathcal{C}}^T \eta) = \begin{bmatrix} \mathcal{C}_l & 0\\ 0 & \mathcal{C}_n(A_{\mathcal{C}_n}^T \eta) \end{bmatrix}, \quad \mathcal{L}(j_{\mathcal{L}}) = \begin{bmatrix} \mathcal{L}_l & 0\\ 0 & \mathcal{L}_n(j_{\mathcal{L}_n}) \end{bmatrix}, \quad g(A_{\mathcal{R}}^T \eta) = \begin{bmatrix} \mathcal{G}_l A_{\mathcal{R}_l}^T \eta\\ g_n(A_{\mathcal{R}_n}^T \eta) \end{bmatrix}.$$

T. Stykel. Model reduction of nonlinear circuit equations - p.8

#### **Replacement of nonlinear elements**



#### **Replacement of nonlinear elements**



### **Replacement of nonlinear elements**



#### **Decoupled system**

Linear RLC equations:  $E \dot{x}_l = A x_l + B u_l$  $y_l = B^T x_l$  with

$$E = \begin{bmatrix} A_C C A_C^T & 0 & 0 \\ 0 & L & 0 \\ 0 & 0 & 0 \end{bmatrix}, \quad A = \begin{bmatrix} -A_R G A_R^T & -A_L & -A_V \\ A_L^T & 0 & 0 \\ A_V^T & 0 & 0 \end{bmatrix}, \quad B = \begin{bmatrix} -A_I & 0 \\ 0 & 0 \\ 0 & -I \end{bmatrix},$$
$$A_C = \begin{bmatrix} A_{Cl} \\ 0 \end{bmatrix}, \quad A_L = \begin{bmatrix} A_{Ll} \\ 0 \end{bmatrix}, \quad A_R = \begin{bmatrix} A_{\mathcal{R}_l} & A_{\mathcal{R}_n,1} & A_{\mathcal{R}_n,2} \\ 0 & -I & I \end{bmatrix}, \quad A_I = \begin{bmatrix} A_{\mathcal{I}} & A_{\mathcal{R}_n,2} & A_{Ln} \\ 0 & I & 0 \end{bmatrix},$$
$$A_V = \begin{bmatrix} A_{\mathcal{V}} & A_{Cn} \\ 0 & 0 \end{bmatrix}, \quad G = \begin{bmatrix} G_l & 0 & 0 \\ 0 & G_1 & 0 \\ 0 & 0 & G_2 \end{bmatrix}, \quad x_I^T = \begin{bmatrix} \eta^T & \eta_Z^T & j_{\mathcal{I}}^T & j_{\mathcal{V}}^T & j_{Cn}^T \\ j_{\mathcal{L}_n}^T & u_{\mathcal{V}}^T & u_{Cn}^T \end{bmatrix};$$

Nonlinear equations:

 $<sup>\</sup>mathcal{C}_n(v_{\mathcal{C}_n})\frac{d}{dt}u_{\mathcal{C}_n} = j_{\mathcal{C}_n}, \quad \mathcal{L}_n(j_{\mathcal{L}_n})\frac{d}{dt}j_{\mathcal{L}_n} = A_{\mathcal{L}_n}^T\eta,$  $j_z = (G_1 + G_2)G_1^{-1}g_n(A_{\mathcal{R}_n}^T\eta) - G_2A_{\mathcal{R}_n}^T\eta$ 

T. Stykel. Model reduction of nonlinear circuit equations - p.12

System G = (E, A, B, C) is balanced if the controllability and observability Gramians X and Y satisfy

 $X = Y = \operatorname{diag}(\sigma_1, \ldots, \sigma_n).$ 

**Idea:** balance the system, i.e., find an equivalence transformation  $(\hat{E}, \hat{A}, \hat{B}, \hat{C}) = (W_b E T_b, W_b A T_b, W_b B, C T_b)$   $= \left( \begin{bmatrix} E_{11} & E_{12} \\ E_{21} & E_{22} \end{bmatrix}, \begin{bmatrix} A_{11} & A_{12} \\ A_{21} & A_{22} \end{bmatrix}, \begin{bmatrix} B_1 \\ B_2 \end{bmatrix}, [C_1, C_2] \right)$ such that  $\hat{X} = \hat{Y} = \text{diag}(\sigma_1, \dots, \sigma_n)$  and truncate the states corresponding to small  $\sigma_i \hookrightarrow \tilde{G} = (E_{11}, A_{11}, B_1, C_1).$ 

**DAES:**  $G(s) = C(sE - A)^{-1}B = G_{sp}(s) + \mathbf{P}(s) \Rightarrow \widetilde{G}(s) = \widetilde{G}_{sp}(s) + \mathbf{P}(s)$ 

T. Stykel. Model reduction of nonlinear circuit equations - p.13

#### **Projected Lur'e equations**

■ If G = (E, A, B, C) is passive, then there exist matrices X = X<sup>T</sup> ≥ 0, J<sub>c</sub>, K<sub>c</sub> and Y = Y<sup>T</sup> ≥ 0, J<sub>o</sub>, K<sub>o</sub> that satisfy
the projected Lur'e equations

 $\begin{aligned} &(A-BC)\,XE^T+EX(A-BC)^T+2P_lBB^TP_l^T=-2K_cK_c^T,\quad X=P_rXP_r^T,\\ &E\,XC^T-P_lBM_0^T=-K_cJ_c^T,\quad I-M_0M_0^T=J_cJ_c^T, \end{aligned}$ 

$$\begin{split} (A-BC)^T Y \, E + E^T Y (A-BC) + 2 P_r^T C^T C P_r &= -2 K_o^T K_o, \quad Y = P_l^T Y P_l, \\ -B^T Y \, E + M_0^T C P_r &= -J_o^T K_o, \qquad I - M_0^T M_0 = J_o^T J_o, \end{split}$$

where  $M_0 = I - 2 \lim_{s \to \infty} C(sE - A + BC)^{-1}B$ ,  $P_r$  and  $P_l$  are the spectral projectors onto the left and right deflating subspaces of the pencil  $\lambda E - A + BC$  corresponding to the finite eigenvalues.

#### **Passivity-preserving BT method**

Given a passive system G = (E, A, B, C).

- 1. Compute  $P_r$ ,  $P_l$ ,  $M_0$ .
- 2. Compute  $X_{\min} = RR^T$ ,  $Y_{\min} = LL^T$  (= solve the Lur'e equations).
- 3. Compute the SVD  $L^T ER = \begin{bmatrix} U_1, U_2 \end{bmatrix} \begin{bmatrix} \Pi_1 \\ \Pi_2 \end{bmatrix} \begin{bmatrix} V_1, V_2 \end{bmatrix}^T$ .
- 4. Compute the reduced-order model

$$\widetilde{E} = \begin{bmatrix} I & 0 \\ 0 & 0 \end{bmatrix}, \qquad \widetilde{A} = \begin{bmatrix} 2W^T A T & \sqrt{2}W^T B C_{\infty} \\ -\sqrt{2}B_{\infty}CT & 2I - B_{\infty}C_{\infty} \end{bmatrix},$$
$$\widetilde{B} = \begin{bmatrix} W^T B \\ -B_{\infty}/\sqrt{2} \end{bmatrix}, \qquad \widetilde{C} = \begin{bmatrix} CT & C_{\infty}/\sqrt{2} \end{bmatrix}$$

with  $I - M_0 = C_{\infty} B_{\infty}$ ,  $W = L U_1 \Pi_1^{-1/2}$  and  $T = R V_1 \Pi_1^{-1/2}$ .

T. Stykel. Model reduction of nonlinear circuit equations - p.15

#### **Properties**

•  $\widetilde{G} = (\widetilde{E}, \widetilde{A}, \widetilde{B}, \widetilde{C})$  is passive

 $\mathbf{S} \quad \widetilde{\mathbf{G}} = (\widetilde{E}, \ \widetilde{A}, \ \widetilde{B}, \ \widetilde{C} \ ) \quad \text{is reciprocal} \quad (\ \widetilde{\mathbf{G}}(s) = \Sigma \ \widetilde{\mathbf{G}}^T(s)\Sigma \ )$ 

- Error bounds:  $\|G\|_{\mathbb{H}_{\infty}} := \sup_{\omega \in \mathbb{R}} \|G(i\omega)\|_2$ 
  - If  $2 \|I + G\|_{\mathbb{H}_{\infty}} (\pi_{\ell_f+1} + \ldots + \pi_{n_f}) < 1$ , then  $\|\widetilde{G} - G\|_{\mathbb{H}_{\infty}} \le 2 \|I + G\|_{\mathbb{H}_{\infty}}^2 (\pi_{\ell_f+1} + \ldots + \pi_{n_f}).$
  - If  $2 \|I + \widetilde{G}\|_{\mathbb{H}_{\infty}} (\pi_{\ell_f+1} + \ldots + \pi_{n_f}) < 1$ , then  $\|\widetilde{G} - G\|_{\mathbb{H}_{\infty}} \le 2 \|I + \widetilde{G}\|_{\mathbb{H}_{\infty}}^2 (\pi_{\ell_f+1} + \ldots + \pi_{n_f}).$

T. Stykel. Model reduction of nonlinear circuit equations - p.16

$$E = \begin{bmatrix} A_C C A_C^T & 0 & 0 \\ 0 & L & 0 \\ 0 & 0 & 0 \end{bmatrix}, \ A - BC = \begin{bmatrix} -A_R G A_R^T - A_I A_I^T & -A_L & -A_V \\ A_L^T & 0 & 0 \\ A_V^T & 0 & -I \end{bmatrix}, \ B = \begin{bmatrix} -A_I & 0 \\ 0 & 0 \\ 0 & -I \end{bmatrix} = C^T$$

Compute  $P_r$  and  $P_l$  using the canonical projectors technique [März'96]

$$\hookrightarrow P_r = \begin{bmatrix} H_5(H_4H_2 - I) & H_5H_4A_{\mathcal{L}}H_6 & 0 \\ 0 & H_6 & 0 \\ -A_{\mathcal{V}}^T(H_4H_2 - I) & -A_{\mathcal{V}}^TH_4A_{\mathcal{L}}H_6 & 0 \end{bmatrix}$$

with  $H_1 = Z_{CRIV}^T A_L L^{-1} A_L^T Z_{CRIV}$ ,  $H_2 = ..., H_3 = Z_C^T H_2 Z_C$ ,  $H_4 = Z_C H_3^{-1} Z_C^T$ ,  $H_5 = Z_{CRIV} H_1^{-1} Z_{CRIV}^T A_L L^{-1} A_L^T - I$ ,  $H_6 = I - L^{-1} A_L^T Z_{CRIV} H_1^{-1} Z_{CRIV}^T A_L$ ,  $Z_C$  and  $Z_{CRIV}$  are basis matrices for ker  $A_C^T$  and ker $[A_C, A_R, A_I, A_V]^T$ .

 $\hookrightarrow$   $P_l = S P_r^T S^T$  with  $S = \text{diag}(I_{n_\eta}, -I_{n_L}, -I_{n_V})$ 

T. Stykel. Model reduction of nonlinear circuit equations – p.17

$$E = \begin{bmatrix} A_C C A_C^T & 0 & 0 \\ 0 & L & 0 \\ 0 & 0 & 0 \end{bmatrix}, \ A - BC = \begin{bmatrix} -A_R G A_R^T - A_I A_I^T & -A_L & -A_V \\ A_L^T & 0 & 0 \\ A_V^T & 0 & -I \end{bmatrix}, \ B = \begin{bmatrix} -A_I & 0 \\ 0 & 0 \\ 0 & -I \end{bmatrix} = C^T$$

• Compute  $P_r$  and  $P_l = S P_r^T S^T$  with  $S = \text{diag}(I_{n_R}, -I_{n_L}, -I_{n_V})$ .

• Compute 
$$M_0 = I - 2 \lim_{s \to \infty} C(sE - A + BC)^{-1}B$$

$$\rightarrow M_0 = \begin{bmatrix} I - 2A_I^T Z H_0^{-1} Z^T A_I & 2A_I^T Z H_0^{-1} Z^T A_V \\ -2A_V^T Z H_0^{-1} Z^T A_I & -I + 2A_V^T Z H_0^{-1} Z^T A_V \end{bmatrix}$$

where  $H_0 = Z^T (A_R G A_R^T + A_I A_I^T + A_V A_V^T) Z$ ,  $Z = Z_C Z'_{RIV-C}$ ,  $Z_{RIV-C}$  is a basis matrix for ker  $[A_R, A_I, A_V]^T Z_C$  and  $[Z_{RIV-C}, Z'_{RIV-C}]$  is nonsingular.

- Compute  $M_0$ ,  $P_r$ ,  $P_l = S P_r^T S^T$  with  $S = \text{diag}(I_{n_R}, -I_{n_L}, -I_{n_V})$ .
- Compute  $X_{\min} = RR^T$ ,  $Y_{\min} = FF^T$  (solve the projected Lur'e equations)

If  $D_0 = I - M_0 M_0^T$  is nonsingular, then the projected Lur'e equations are equivalent to the projected Riccati equation

- $$\begin{split} (A BC)XE^T + EX(A BC)^T + 2\,P_l BB^T P_l^T \\ &+ 2(EXC^T P_l BM_0^T)D_0^{-1}(EXC^T P_l BM_0^T) = 0, \quad X = P_r XP_r^T \end{split}$$
  - $\hookrightarrow$  compute a low-rank approximation  $X_{\min} \approx \widetilde{R}\widetilde{R}^T$ ,  $\widetilde{R} \in \mathbb{R}^{n,k}$ ,  $k \ll n$ , using the generalized low-rank Newton method [Benner/St.'10]
  - $\hookrightarrow \ Y_{\min} = S X_{\min} S^T \approx S \widetilde{R} \widetilde{R}^T S^T = \widetilde{F} \widetilde{F}^T$
  - $\rightarrow D_0$  is nonsingular, if the circuit contains neither CVI-loops except for C-loops nor LIV-cutsets except for L-cutsets

T. Stykel. Model reduction of nonlinear circuit equations – p.19

- Compute  $M_0$ ,  $P_r$ ,  $P_l = S P_r^T S^T$  with  $S = \text{diag}(I_{n_R}, -I_{n_L}, -I_{n_V})$ .
- **Solution** Compute the SVD of  $\tilde{F}^T E \tilde{R}$ 
  - $\hookrightarrow \widetilde{F}^T E \widetilde{R} = \widetilde{R}^T S E \widetilde{R} \quad \text{is symmetric}$
  - $\hookrightarrow$  compute the EVD  $\tilde{R}^T SE\tilde{R} = \begin{bmatrix} U_1, U_2 \end{bmatrix} \begin{bmatrix} \Lambda_1 \\ \Lambda_2 \end{bmatrix} \begin{bmatrix} U_1, U_2 \end{bmatrix}^T$  instead of the SVD
  - $\hookrightarrow W = S\widetilde{R}U_1|\Lambda_1|^{-1/2} \text{ and } T = \widetilde{R}U_1|\Lambda_1|^{-1/2}\operatorname{sign}(\Lambda_1) \text{ with} \\ |\Lambda_1| = \operatorname{diag}(|\lambda_1|, \dots, |\lambda_{\ell_f}|), \quad \operatorname{sign}(\Lambda_1) = \operatorname{diag}(\operatorname{sign}(\lambda_1), \dots, \operatorname{sign}(\lambda_{\ell_f}))$

- Compute  $M_0$ ,  $P_r$ ,  $P_l = S P_r^T S^T$  with  $S = \text{diag}(I_{n_R}, -I_{n_L}, -I_{n_V})$ .
- Compute  $X_{\min} \approx \widetilde{R}\widetilde{R}^T$ .
- Compute the EVD  $\tilde{R}^T SE\tilde{R} = \begin{bmatrix} U_1, U_2 \end{bmatrix} \begin{bmatrix} \Lambda_1 \\ \Lambda_2 \end{bmatrix} \begin{bmatrix} U_1, U_2 \end{bmatrix}^T$  and  $W = S\tilde{R}U_1 |\Lambda_1|^{-1/2}, \quad T = \tilde{R}U_1 |\Lambda_1|^{-1/2} \operatorname{sign}(\Lambda_1).$
- Compute  $B_{\infty}$  and  $C_{\infty}$  such that  $C_{\infty}B_{\infty} = I M_0$ 
  - $\hookrightarrow (I M_0)\Sigma$  with  $\Sigma = \text{diag}(I_{n_I}, -I_{n_V})$  is symmetric
  - $\hookrightarrow$  compute the EVD  $(I M_0)\Sigma = U_0 \Lambda_0 U_0^T$
  - $\hookrightarrow B_{\infty} = \operatorname{sign}(\Lambda_0) |\Lambda_0|^{1/2} U_0^T \Sigma$  and  $C_{\infty} = U_0 |\Lambda_0|^{1/2}$

T. Stykel. Model reduction of nonlinear circuit equations – p.21

#### **PABTECL** algorithm

- Compute  $M_0$ ,  $P_r$ ,  $P_l = S P_r^T S^T$  with  $S = \text{diag}(I_{n_R}, -I_{n_L}, -I_{n_V})$ .
- Compute  $X_{\min} \approx \widetilde{R}\widetilde{R}^T$ .
- Compute the EVD  $\tilde{R}^T SE\tilde{R} = \begin{bmatrix} U_1, U_2 \end{bmatrix} \begin{bmatrix} \Lambda_1 \\ \Lambda_2 \end{bmatrix} \begin{bmatrix} U_1, U_2 \end{bmatrix}^T$  and  $W = S\tilde{R}U_1 |\Lambda_1|^{-1/2}, \quad T = \tilde{R}U_1 |\Lambda_1|^{-1/2} \operatorname{sign}(\Lambda_1).$
- Compute the EVD  $(I M_0)\Sigma = U_0\Lambda_0 U_0^T$  with  $\Sigma = \text{diag}(I_{n_{\mathcal{I}}}, -I_{n_{\mathcal{V}}})$ and  $B_{\infty} = \text{sign}(\Lambda_0)|\Lambda_0|^{1/2}U_0^T\Sigma$ ,  $C_{\infty} = U_0|\Lambda_0|^{1/2}$ .

Compute the reduced-order model

$$\widetilde{E} = \begin{bmatrix} I & 0 \\ 0 & 0 \end{bmatrix}, \qquad \widetilde{A} = \frac{1}{2} \begin{bmatrix} 2W^T A T & \sqrt{2}W^T B C_{\infty} \\ -\sqrt{2}B_{\infty}CT & 2I - B_{\infty}C_{\infty} \end{bmatrix},$$
$$\widetilde{B} = \begin{bmatrix} W^T B \\ -B_{\infty}/\sqrt{2} \end{bmatrix}, \qquad \widetilde{C} = \begin{bmatrix} CT, \ C_{\infty}/\sqrt{2} \end{bmatrix}.$$

#### Recoupling

Linear reduced-order model:

$$\widetilde{E}\,\dot{\widetilde{x}}_{l} = \widetilde{A}\,\widetilde{x}_{l} + \left[\widetilde{B}_{1},\,\widetilde{B}_{2},\,\widetilde{B}_{3},\,\widetilde{B}_{4},\,\widetilde{B}_{5}\right]u_{l},\\ \widetilde{V}_{l} = \begin{bmatrix}\widetilde{C}_{1}\\\widetilde{C}_{2}\\\widetilde{C}_{3}\\\widetilde{C}_{4}\\\widetilde{C}_{5}\end{bmatrix}\widetilde{x}_{l} \approx y_{l} = \begin{bmatrix}-A_{\mathcal{R}_{n}}^{T}\eta\\-A_{\mathcal{R}_{n}}^{T}\eta+G_{1}^{-1}g_{n}(A_{\mathcal{R}_{n}}^{T}\eta)\\-A_{\mathcal{L}_{n}}^{T}\eta\\-j_{\mathcal{V}}\\-j_{\mathcal{C}_{n}}\end{bmatrix}$$

Nonlinear equations:

 $\mathcal{C}_n(v_{\mathcal{C}_n})\frac{d}{dt}u_{\mathcal{C}_n} = j_{\mathcal{C}_n},$  $\mathcal{L}_n(j_{\mathcal{L}_n})\frac{d}{dt}j_{\mathcal{L}_n} = A_{\mathcal{L}_n}^T\eta,$  $j_z = (G_1 + G_2)G_1^{-1}g_n(A_{\mathcal{R}_n}^T\eta) - G_2A_{\mathcal{R}_n}^T\eta$ 

T. Stykel. Model reduction of nonlinear circuit equations – p.23

#### **Reduced-order nonlinear system**

We obtain the reduced-order system

$$\widetilde{\mathcal{E}}(\widetilde{x})\,\dot{\widetilde{x}} = \widetilde{\mathcal{A}}\,\widetilde{x} + \widetilde{f}(\widetilde{x}) + \widetilde{\mathcal{B}}\,u$$
$$\widetilde{y} = \widetilde{\mathcal{C}}\,\widetilde{x}$$

with

$$\widetilde{\mathcal{E}}(\widetilde{x}) = \begin{bmatrix} \widetilde{E} & 0 & 0 & 0 \\ 0 & \mathcal{L}_n(\widetilde{j}_{\mathcal{L}_n}) & 0 & 0 \\ 0 & 0 & \mathcal{C}_n(\widetilde{u}_{\mathcal{C}_n}) & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}, \quad \widetilde{\mathcal{A}} = \begin{bmatrix} \widetilde{A} + \widetilde{B}_2(G_1 + G_2)\widetilde{C}_2 & \widetilde{B}_3 & \widetilde{B}_5 & \widetilde{B}_2G_1 \\ -\widetilde{C}_3 & 0 & 0 & 0 \\ -\widetilde{C}_5 & 0 & 0 & 0 \\ -G_1\widetilde{C}_2 & 0 & 0 & -G_1 \end{bmatrix}, \\ \widetilde{\mathcal{B}} = \begin{bmatrix} \widetilde{B}_1 & \widetilde{B}_4 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix}, \quad \widetilde{f}(\widetilde{x}) = \begin{bmatrix} 0 \\ 0 \\ 0 \\ g_n(\widetilde{u}_{\mathcal{C}_n}) \\ 0 \end{bmatrix}, \quad \widetilde{x} = \begin{bmatrix} \widetilde{x}_l \\ \widetilde{j}_{\mathcal{L}_n} \\ \widetilde{u}_{\mathcal{R}_n} \\ \widetilde{u}_{\mathcal{R}_n} \end{bmatrix}.$$

**Remark:** If  $n_{C_n} = 0$  and  $n_{L_n} = 0$ , then passivity is preserved and under some additional topological conditions we have the error bound  $\|\widetilde{y} - y\|_2 \le c(\pi_{\ell_f} + \ldots + \pi_{n_f})(\|u\|_2 + \|\widetilde{y}\|_2)$ . [Heinkenschloss/Reis'09]

#### **Example: linear RLC circuit**



### **Example: nonlinear circuit**



T. Stykel. Model reduction of nonlinear circuit equations - p.26

## **Conclusions and future work**

- Model reduction of nonlinear circuit equations
  - topology based partitioning
  - balancing-related model reduction of linear subsystems with preservation of passivity and computable error bounds
- Exploiting the structure of MNA matrices E, A, B, C
  - use graph algorithms for computing the basis matrices
  - use modern numerical linear algebra algorithms for solving large-scale projected Riccati/Lyapunov equations
- $\hookrightarrow$  MATLAB Toolbox PABTEC
  - Preservation of passivity and error bounds for general circuits
  - Numerical solution of large-scale Lur'e equations